

ECEN2350

Project2-Report

Chengming Li

1. Project Statement

In this project, we are going to learn the synchronous design techniques, and to create testbenches that simulate this synchronous design. Generally, we are designing a calendar that displays the days of year, the month of years and the days of month on the De10-lite board. Also, for the calendar, we should be able to display the days of leap year, the month of leap years and the days of month. Moreover, we need to create a clock divider to slow down the frequency of updating. There are 2 frequencies we need to get. One is 2Hz and another one is 5Hz. And we need to Connect the display clock to LEDR[0] so we can see the LED blink at the display clock rate. At the end of the design, we should be able to switch the frequency of the clock by pressing the button KEY[1].

2. Theory of operation

In this project, we should know how to create a clock that starts the counting automatically. And the data changes at the positive edge of the tick. Also, for each clock, we must include the RESET signal, which makes effects at the negative edge of the tick, as the highest priority in the clock. In our design, the RESET signal is active low, which means it is logic true when it is in the 0 state. Moreover, we should notice that we are using non-blocking assignments (\leq) at most times. A non-blocking assignment means that statements are evaluated using the variable values when the always or initial block was entered.

In the first requirement, we should design a counter that goes from 1 to 99 with a RESET signal, which represents the first 99 days of the year. For convenience, I create two counters, countMSB and countLSB. Each counter is 4 bit wide, so it only counts from 4'b0 to 4'b1001. And when countLSB counts to 9, countMSB will add 1 and countLSB roll back to 0. At the end, when they both count to 99, they will roll over. CountMSB will display at HEX5 and CountLSB will display at HEX4

```

Project2 > Source > counterBCD.v
1  module counterBCD(
2      input clock, reset_n,
3      output reg [3:0] countLSB, countMSB
4      //output wire [7:0] HEX5, HEX4
5  );
6
7
8  always @(posedge clock, negedge reset_n )
9  begin
10     if (reset_n == 0)
11     begin
12         countLSB <= 1;           // Reset LEB = 1
13         countMSB <= 0;          // Reset MSB = 0;
14     end
15
16     else if (countLSB != 9)
17     begin
18         countLSB <= countLSB + 1;    //LSB counter
19     end
20     else if (countMSB == 9 && countLSB==9 )    // Roll over / same as reset
21     begin
22         countLSB <= 1;
23         countMSB <= 0;
24     end
25
26     else
27     begin
28         if(countLSB == 9)begin           //MSB counter
29             countMSB <= countMSB+1;
30         end
31         countLSB <=0;                    // When LSB count to 9, roll over
32     end
33
34     end
35 endmodule
36

```

Figure1. 0-99 counter

The second major requirement, we should code a clock divider which could slow down the frequency of clock source so that we can see the updating of numbers in the HEX display. Since we are using 10M hz clock source, we should create a 23 bit wide clock divider to slow it down. So, we could get the expected clock frequency by this divider. In my design, I create a parameter divide_by which is used to slow down the clock to the expected frequency. Divide_by is 0 inside of my clock_divider file for convenience of instantiation. When I instantiate this clock_divider block, I could simply put #(expected value) in the line of my instantiation. #(expected value) will take the place of parameter divide_by inside of the clock_divider module.

```

Project2 > Source > clock_divider.v
1  module clock_divider(
2      input clock_in, reset_n,
3      output reg clock_out
4      //output [9:0] LEDR
5  );
6
7      reg [22:0] clock_divider;
8      //parameter divide_by = 5_000_000;
9      parameter divide_by = 0;
10
11     always@(posedge clock_in, negedge reset_n)
12     begin
13         if(~reset_n)
14         begin
15             clock_out = 0;
16             clock_divider = 0;
17         end
18         else
19         begin
20             if(clock_divider != divide_by-1)begin
21                 clock_divider <= clock_divider+1;
22             end
23             else begin
24                 clock_divider <= 0;
25                 clock_out = ~clock_out;
26             end
27         end
28     end
29
30 endmodule

```

Figure 2. Clock_divider

```

clock_divider #(5_000_000)F2hz (.reset_n(reset_n),.clock_in(ADC_CLK_10),.clock_out(clock2HZ));
|
clock_divider #(2_000_000) F5hz (.reset_n(reset_n),.clock_in(ADC_CLK_10),.clock_out(clock5HZ));

```

Figure 3. Clock_divider instantiation

The last requirement is displaying the months of year and the days of month in HEX3, HEX2, HEX1 and HEX0. In this block, I make a binary to decimal decoder, which could concatenate countMSB and countLSB to decimal in binary. With this binary_value, we could make multiple if statements to determine which month are the counter in at that time. So we could assign the month number to month displays.

Moreover, in another block, I create a simple calculation to calculate the days of month by multiple if statements to determine the days_MSB and the days_LSB.

```
1  module DDMM1(  
2  input wire  [3:0] MSB,LSB,  
3  //input  clock, reset_n,  
4  input [9:0] SW,  
5  output reg[4:0] DD,  
6  output reg[3:0] MM,MM_MSB  
7  
8  );  
9  wire [7:0] binary_value;  
10 assign binary_value = (MSB[3:0]*10)+({4'b0,LSB[3:0]}); // 4 bits to decimal  
11  
12  
13  
14 wire leap_year;  
15 assign leap_year = SW[9];  
16  
17  
18 always@(*)  
19 begin  
20  
21     if (binary_value <= 31) begin // January  
22         MM <= 1;  
23         DD <= binary_value; //  
24         MM_MSB = 0;  
25     end  
26     else if (binary_value <= 31+28+leap_year) begin //Feb  
27         MM <= 2;  
28         DD <= binary_value - 31;  
29         MM_MSB = 0;  
30     end  
31     else if (binary_value <= 31+28+leap_year+31) begin // March  
32         MM <= 3;  
33         DD <= binary_value - 31-28-leap_year;  
34         MM_MSB = 0;  
35     end  
36     else begin // April  
37         MM <= 4;  
38         DD <= binary_value-31-28-leap_year-31;  
39         MM_MSB = 0;  
40     end  
41 end  
42
```

Figure 4. DDMM_month

```

module DD_MSB_LSB(
input [4:0] DD,
output reg [3:0] DD_MSB,DD_LSB

);

always@(DD)
begin
    if (DD < 10) begin
        DD_MSB = 0;
        DD_LSB = DD;
    end

    else if (DD< 20)begin
        DD_MSB = 1;
        DD_LSB = DD-10 ;
    end
    else if (DD <30) begin
        DD_MSB = 2;
        DD_LSB = DD-20;
    end
    else
    begin
        DD_MSB = 3;
        DD_LSB = DD-30;
    end
end

endmodule

```

Figure 5. DD_MSB_LSB

3. Hierarchy of My project source files

MAX 10: 10M50DAF484C7G
Project2
counterBCD:C1
DDMM1:D1
DD_MSB_LSB:D2
clock_divider:F2hz
clock_divider:F5hz
decoder:H0
decoder:H1
decoder:H2
decoder:H3
decoder:H4
decoder:H5

Figure 6. Hierarchy

4. Block diagram

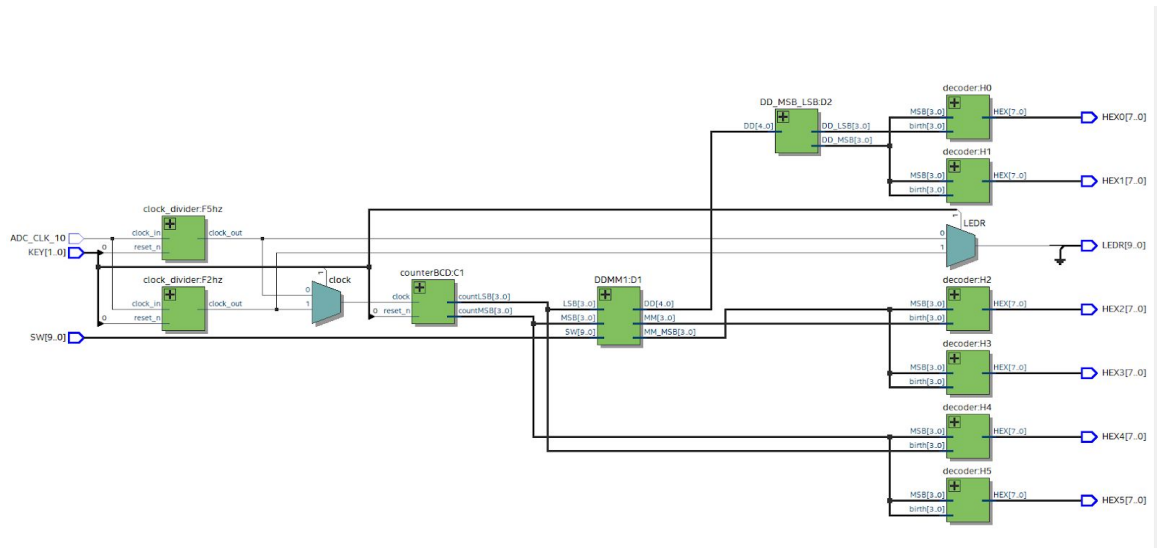


Figure 7. Block diagram

5. Description of Testbench operation

```

2 `timescale 1 ns / 100 ps
3 module tb_Project2();
4
5
6 reg [1:0]KEY;
7 reg [9:0] SW;
8 reg ADC_CLK_10;
9
10 wire [7:0] HEX5,HEX4,HEX3,HEX2,HEX1,HEX0;
11 wire [9:0] LEDR;
12
13 Project2 top (.ADC_CLK_10(ADC_CLK_10),.KEY(KEY),.SW(SW),.HEX5(HEX5),.HEX4(HEX4),.HEX3(HEX3),.HEX2(HEX2),.HEX1(HEX1),.HEX0(HEX0),.LEDR(LEDR));
14
15 always #10 ADC_CLK_10 = ~ADC_CLK_10;
16
17 initial
18 begin
19     $dumpfile("tb_top.vcd");$dumpvars;
20     ADC_CLK_10 = 0; SW[9]=0; KEY[0] = 0;KEY[1] =1;
21
22     #100 KEY[0] = 1;
23     #20000;
24     #1000 SW[9] = 1;
25     #3000;
26     #100 $finish;
27 end
28

```

Figure 8. top_tb.v

In the testbench of top.v module, I only instantiate the top module which is Project2 in line 13. Project 2.v includes all the counter, clock divider and decoder modules. For the simulation of a clock like this, we must create an always block to flip the state of clock source in each 10 times timescale delay, like in line 15, to start the counting. Then, within the initial clock, we must initialize everything that is related to our operation, such as clock source, SW and SW, which could make the simulation work properly. Moreover, we also need to reset the clock at the beginning of the counter in order to clean everything before the counting. For the counting, we simply put #(times) to start it. During some delay, we also could simulate some operations we want, like flipping the switch, pressing the KEY, etc.

 


Figure 9. Gtkwave_top

The figure above shows the beginning of the counter, which includes the days of year, months of year and the days of month with the RESET signal.

```
VCD info: dumpfile tb_DDMM.vcd opened for output.
  0 binary_value = 1, DD = 1 , DD_MSB = 0, DD_LSB = 1 , MM = 1
 30 binary_value = 2, DD = 2 , DD_MSB = 0, DD_LSB = 2 , MM = 1
 50 binary_value = 3, DD = 3 , DD_MSB = 0, DD_LSB = 3 , MM = 1
 70 binary_value = 4, DD = 4 , DD_MSB = 0, DD_LSB = 4 , MM = 1
 90 binary_value = 5, DD = 5 , DD_MSB = 0, DD_LSB = 5 , MM = 1
110 binary_value = 6, DD = 6 , DD_MSB = 0, DD_LSB = 6 , MM = 1
130 binary_value = 7, DD = 7 , DD_MSB = 0, DD_LSB = 7 , MM = 1
150 binary_value = 8, DD = 8 , DD_MSB = 0, DD_LSB = 8 , MM = 1
170 binary_value = 9, DD = 9 , DD_MSB = 0, DD_LSB = 9 , MM = 1
190 binary_value = 10, DD = 10 , DD_MSB = 1, DD_LSB = 0 , MM = 1
210 binary_value = 11, DD = 11 , DD_MSB = 1, DD_LSB = 1 , MM = 1
230 binary_value = 12, DD = 12 , DD_MSB = 1, DD_LSB = 2 , MM = 1
250 binary_value = 13, DD = 13 , DD_MSB = 1, DD_LSB = 3 , MM = 1
270 binary_value = 14, DD = 14 , DD_MSB = 1, DD_LSB = 4 , MM = 1
290 binary_value = 15, DD = 15 , DD_MSB = 1, DD_LSB = 5 , MM = 1
310 binary_value = 16, DD = 16 , DD_MSB = 1, DD_LSB = 6 , MM = 1
330 binary_value = 17, DD = 17 , DD_MSB = 1, DD_LSB = 7 , MM = 1
350 binary_value = 18, DD = 18 , DD_MSB = 1, DD_LSB = 8 , MM = 1
370 binary_value = 19, DD = 19 , DD_MSB = 1, DD_LSB = 9 , MM = 1
390 binary_value = 20, DD = 20 , DD_MSB = 2, DD_LSB = 0 , MM = 1
410 binary_value = 21, DD = 21 , DD_MSB = 2, DD_LSB = 1 , MM = 1
430 binary_value = 22, DD = 22 , DD_MSB = 2, DD_LSB = 2 , MM = 1
450 binary_value = 23, DD = 23 , DD_MSB = 2, DD_LSB = 3 , MM = 1
```

Figure 10. Txt_output

Figure 10 shows the text output in the terminal which shows the counting of days of year (DD or binary_value), months of year(MM) and the days of month (DD_MSB and DD_LSB). This simulation uses another testbench module shown in Figure 11.


```

Project2 > Source > # tb_DDMM.v
1 `timescale 1 ns / 100 ps
2 module tb_DDMM();
3
4 reg clock = 0;
5
6 wire reset_n;
7 reg [1:0] KEY;
8 reg [9:0] SW;
9
10 wire [3:0] MSB_LSB; // day of years
11 wire [3:0] MM_DD_MSB_DD_LSB_MM_MSB;
12 wire [4:0] DD;
13 wire [7:0] binary_value;
14 assign binary_value = (MSB[3:0]*10)+({4'b0,LSB[3:0]});
15 counterBCD C1(.clock(clock),.reset_n(reset_n),.countMSB(MSB),.countLSB(LSB));
16
17 DD_MSB_LSB D2(.DD(DD),.DD_MSB(DD_MSB),.DD_LSB(DD_LSB));
18 DDMM1 D1(.MSB(MSB),.LSB(LSB),.DD(DD),.MM(MM),.SW(SW),.MM_MSB(MM_MSB));
19
20
21
22
23 assign reset_n = KEY[0]? KEY[0]:KEY[0];
24
25 always#10 clock = ~clock;
26
27 initial
28 begin
29     $dumpfile("tb_DDMM.vcd");
30     $dumpvars;
31     KEY[0] = 0; // Reset/ initialized MSB and LSB/ KEY[0] is pressed
32     SW[9:0] = 10'b0;
33
34     #10 KEY[0] = 1; // KEY[0] is not pressed after 10ns delay
35     #2200; // clock 110
36
37
38
39     #10 $finish;
40 end
41
42
43 initial
44 begin
45     $monitor($time, " binary_value = %d, DD = %d, DD_MSB = %d, DD_LSB = %d, MM = %d", binary_value,DD, DD_MSB,DD_LSB,MM );
46 end
47 endmodule

```

Figure 11. tb_DDMM.v

6. Summary

This project gives me a better understanding of clock and simulation.

Like, I understand the syntax of creating the clock testbench and clock. Also, the gtkwave simulation helps me to better visualize the process of data transmitting, such as the positive edge and negative edge. Meanwhile, this project also teaches me how to create a clock divider to slow down the clock.

I'm feeling ok with this project because everything is working properly on my board. Especially, the leap year counting is working whenever I flip the SW[9] during the counting. There is 1 day difference whenever the SW[9] is flipped. And, the KEY[1] is also working properly whenever I want to accelerate the counting of the clock. Last but not least, this project really gives me a better understanding of all the concepts about timer or clock, and the ability to read the gtkwave output.

